

Jharkhand University of Technology, Ranchi**B.Tech. 2nd Semester Examination, 2019****Subject : Basic Electrical Engineering****Subject Code : ESC-101****Time Allowed : 3 Hours****Full Marks : 70***Candidates are required to give their answers in their own words as far as practicable.**The figures in the margin indicate full marks.**Answer any five questions.***1. Choose the correct answer:****2×7=14**

- (i) You have to replace 1500Ω resistor in radio. You have no 1500Ω resistor but have several 1000Ω ones which you would connect
- (a) two in parallel.
 - (b) two in parallel and one in series.
 - (c) three in series.
 - (d) three in parallel.
- (ii) In any AC circuit always
- (a) apparent power is more than actual power.
 - (b) reactive power is more than apparent power.
 - (c) actual power is more than reactive power.
 - (d) reactive power is more than actual power.
- (iii) Power factor of an inductive circuit is usually improved by connecting capacitor to it in
- (a) parallel
 - (b) series
 - (c) Either (a) or (b)
 - (d) None of the above
- (iv) A 3 phase 440V, 50 Hz induction motor has 4% slip. The frequency of rotor emf will be
- (a) 200 Hz
 - (b) 50 Hz
 - (c) 0.2 Hz
 - (d) 2 Hz

$$f_r = 4$$

$$f_r = \frac{s \times 50}{100} = \frac{4 \times 50}{100} = 2 \text{ Hz}$$

(v) A transformer core is laminated to

- (a) reduce hysteresis loss.
- (b) reduce eddy current losses.
- (c) reduce copper loss.
- (d) reduce all above losses.

(vi) A star connected load has three equal impedance each of $(40 + j30)\Omega$. If the line current is 5A then value of line voltage is

- (a) 250 volt
- (b) $\frac{250}{\sqrt{3}}$ volt
- (c) $250\sqrt{3}$ volt
- (d) 200 volt

(vii) The main function of a fuse is to


- (a) protect the line.
- (b) open the circuit.
- (c) protect the appliance.
- (d) prevent excessive currents.

Or, 6

✓ (a) State and explain superposition theorem.

✓ (b) For the following circuit find V_1 and V_2 using superposition theorem. (8)

6+8=14

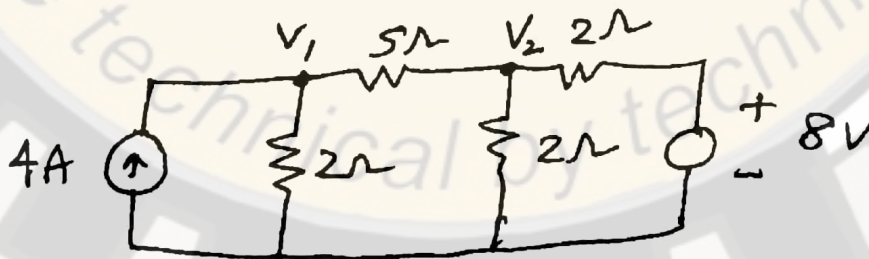

2. (a) State and explain Thevenin's and Norton's theorem. 6

(b) Find the Thevenin's equivalent and Norton's equivalent across ab of the circuit given below: (8)

6+8=14

2Ω

a

(8)

3. (a) Explain about 3 phase balanced and unbalanced load.
 (b) Establish the relationship between line voltage and phase voltage for star connection.
 (c) A two element series circuit consumes 700W and has a power factor 0.707 leading. If applied voltage is $v(t) = 141.4 \sin(314t + 30^\circ)$ volt, find the circuit constant. $2+5+7=14$

4. (a) Explain principle of operation of a transformer. Derive the expression for the emf induced in a transformer. 7

- (b) A 100 kVA, 2200/440V single phase transformer has $r_1 = 0.3\Omega$, $x_1 = 1.1\Omega$
 $r_2 = 0.01\Omega$, $x_2 = 0.035\Omega$

Calculate: (i) The equivalent impedance of the transformer referred to primary side. (7)

(ii) Total copper loss. $7+7=14$

5. (a) Explain working principle of a 3 phase induction motor. Discuss the torque slip characteristics of the motor. 7

- (b) A 3 phase 50 Hz, 4 pole induction motor has a slip of 4%, calculate speed of the motor, frequency of rotor emf. If the rotor has a resistance of 1Ω and standstill reactance of 4Ω . Calculate the power factor of the rotor (i) at standstill and (ii) at a speed of 1400 rpm. $7+7=14$ (7)

6. (a) Explain B-M characteristics of a magnetic material.
 (b) Describe regulation and efficiency of a transformer.
 (c) Explain different methods of speed control of 3-phase induction motor.
 (d) Explain the construction of synchronous generator.
 (e) Why earthing is done? $3+3+3+3+2=14$

7. Write short notes on *any three* of the following: $4+5+5=14$

- (a) Time domain analysis of RL circuit
 (b) Starting methods of 3 phase induction motor
 (c) Auto transformer 4
 (d) Equivalent circuit of a single phase transformer 5
 (e) DC/DC Buck-Boost converter 5